


Chapter 4

Building a simple ALU to support MIPS arithmetic instructions

**Extra material (Appendix C.5 under
Oncourse:resources)**

Introduction

 
- What's up ahead:
 - Implementing the Processor Architecture
 - Design simple ALU to support MIPS arithmetic/logic instructions



MIPS ALU requirements

- **add, addu, sub, subu, addi, addiu**
 - **2's complement adder/sub with overflow detection**
- **and, or, andi, ori, xor, xori, nor**
 - **Logical and, logical or, xor, nor**
- **slt, sltu, slti, sltiu (set less than)**
 - **→ 2's complement adder with inverter, check sign bit of result**
- **ALU we will design supports these**

MIPS arithmetic instruction format

 

<u>Type</u>	<u>op</u>	<u>funct</u>
addi	10	xx
addiu	11	xx
slti	12	xx
sltiu	13	xx
andi	14	xx
ori	15	xx
xori	16	xx
lui	17	xx


<u>Type</u>	<u>op</u>	<u>funct</u>
add	00	40
addu	00	41
sub	00	42
subu	00	43
and	00	44
or	00	45
xor	00	46
nor	00	47

<u>Type</u>	<u>op</u>	<u>funct</u>
	00	50
	00	51
slt	00	52
sltu	00	53

Octal values

Design trick

 
- take pieces you know and try to put them together.
 - We will design the processor one bit at a time.
 - We will design the modules of the processor and put them together.
 - Multiplexer: one component used to put modules together
- 2-to-1 Multiplexor (**MUX**)
 - $Y = S ? I1 : I0$



An ALU (arithmetic logic unit)

- Let's build an ALU to support the `and` and `or` instructions
 - we'll just build a 1 bit ALU, and use 32 of them

 $operation = \begin{cases} 0 & \text{AND} \\ 1 & \text{OR} \end{cases}$




	op	a	b	res
AND	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	1
OR	1	0	0	0
	1	0	1	1
	1	1	0	1
	1	1	1	1


- Possible Implementation (sum-of-products):

$$result = \overline{op} \cdot a \cdot b + op \cdot (a + b)$$

Op would be the select (S) bit for MUX

 

 
Partial ALU supporting **and** and **or**



op	$result$
0	$I_0 = a \cdot b$
1	$I_1 = a + b$

Different Implementations

 - Not easy to decide the “best” way to build something
 - Don't want too many inputs to a single gate
 - Don't want to have to go through too many gates
 - for our purposes, ease of comprehension is important
- Let's look at a 1-bit ALU for addition:




$$c_{out} = a b + a c_{in} + b c_{in}$$
$$sum = a \oplus b \oplus c_{in}$$

Full Adder

- How could we build a 1-bit ALU for add, and, and or?
- How could we build a 32-bit ALU?

Larger multiplexors

 - **4-to-1 MUX : 2 select bits; selects one of 4 inputs**




$S_1 S_0$	Y
00	I_0
01	I_1
10	I_2
11	I_3

Building a 32 bit ALU


Opcode = 0 ➔ AND

Opcode = 1 ➔ OR

Opcode = 2 ➔ ADD


 


32-bit
ALU

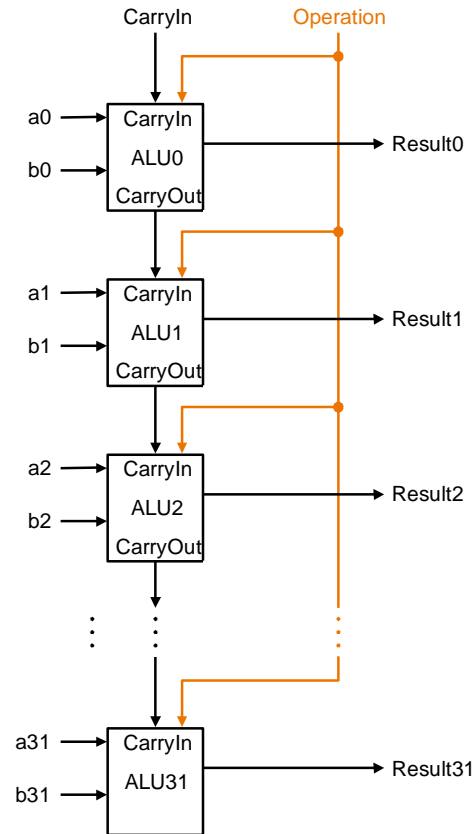

What about subtraction ($a - b$) ?

  - Two's complement approach: just **negate** b and add.
- How do we negate (not invert)?
Carry-in = Binvert for LSB
Call it bnegate (1 control bit)
- A very clever solution:




NOR operation

- We can add NOR operation by using DeMorgan's law:

$$(a + b)' = a' \cdot b'$$

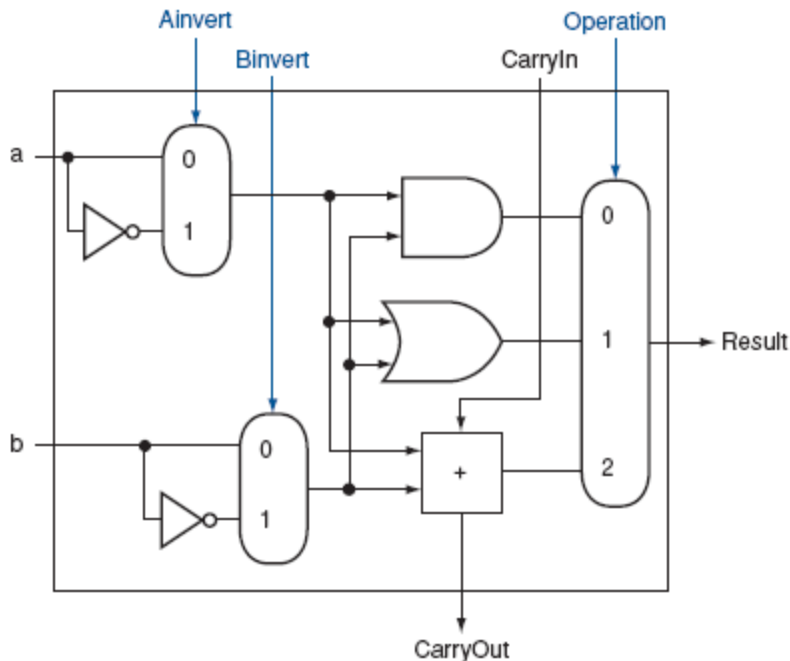- We can easily add this using the existing AND gate with inverters to the inputs:



To implement NOR
Ainvert=1
Binvert=1
Op=0 (and)

Tailoring the ALU to the MIPS

- Need to support the set-on-less-than instruction (slt)
 - remember: slt is an arithmetic instruction
 - produces a 1 if $rs < rt$ and 0 otherwise
 - use subtraction: $(a-b) < 0$ implies $a < b$
- Need to support test for equality (beq \$t5, \$t6, \$t7)
 - use subtraction: $(a-b) = 0$ implies $a = b$


Supporting slt

- Can we figure out the idea?


$$Less = \begin{cases} 1 & \text{if } a < b \\ 0 & \text{if } a \geq b \end{cases}$$

$$= \begin{cases} 1 & \text{if } (a-b) < 0 \\ 0 & \text{if } (a-b) \geq 0 \end{cases}$$

Sign bit

 


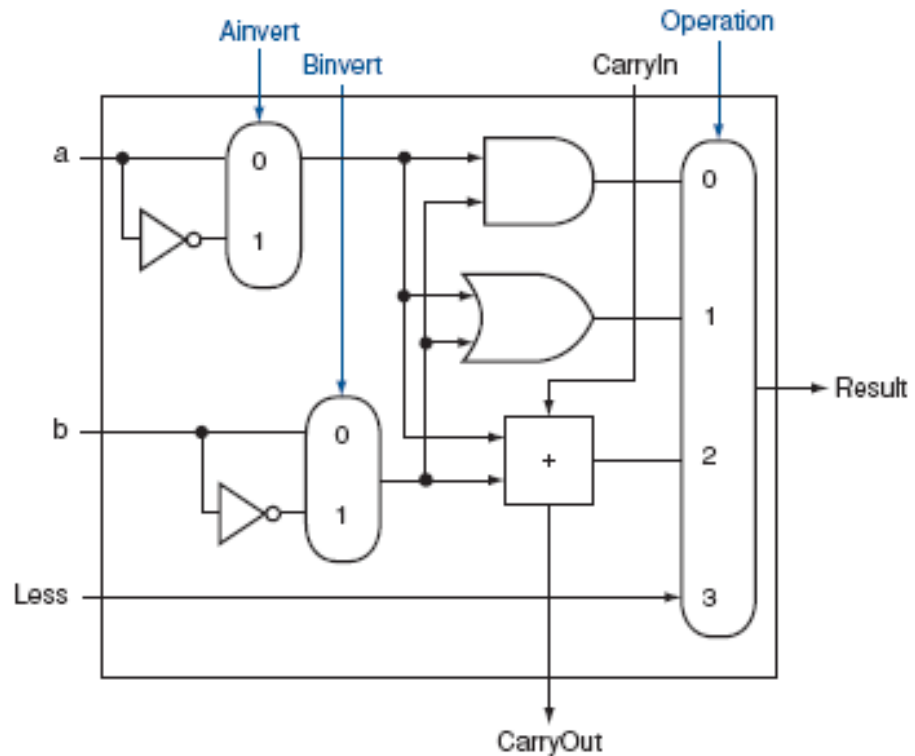LSB of the word is
set to 1 if less=1; all
the other bits are always
set to 0 Op for slt=3



Supporting overflow detection

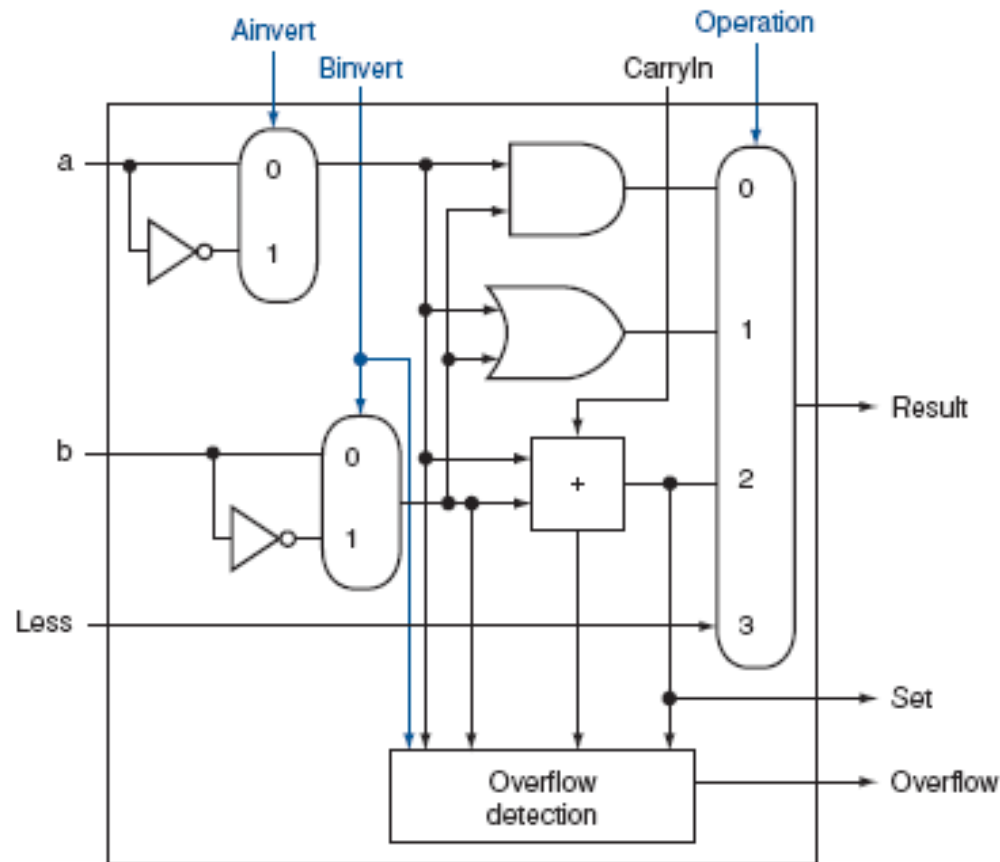
- Since we need a special ALU hardware for the **MSB**, we might as well add the overflow logic.




Overflow circuitry
is done only for **MSB**

Overflow Detection Logic

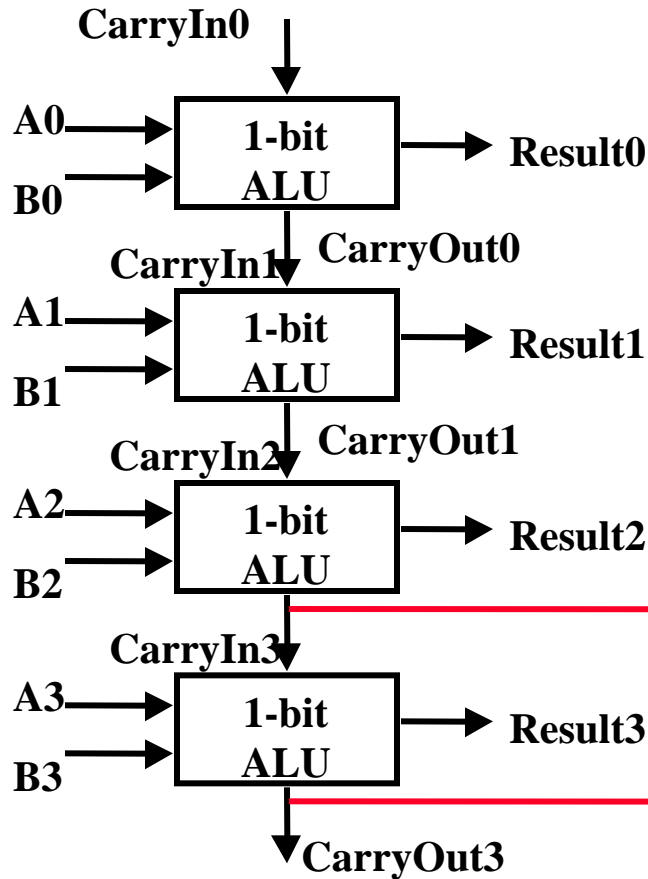- Remember: **Overflow = Carry into MSB \oplus Carry out of MSB**
 - For a n-bit ALU: **Overflow = CarryIn[n - 1] XOR CarryOut[n - 1]**




X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

 

Supporting slt

LSB bit gets fed
from the Set result
of the MSB which
is the sign bit of
(a-b)

All less bits are
always = 0
except LSB

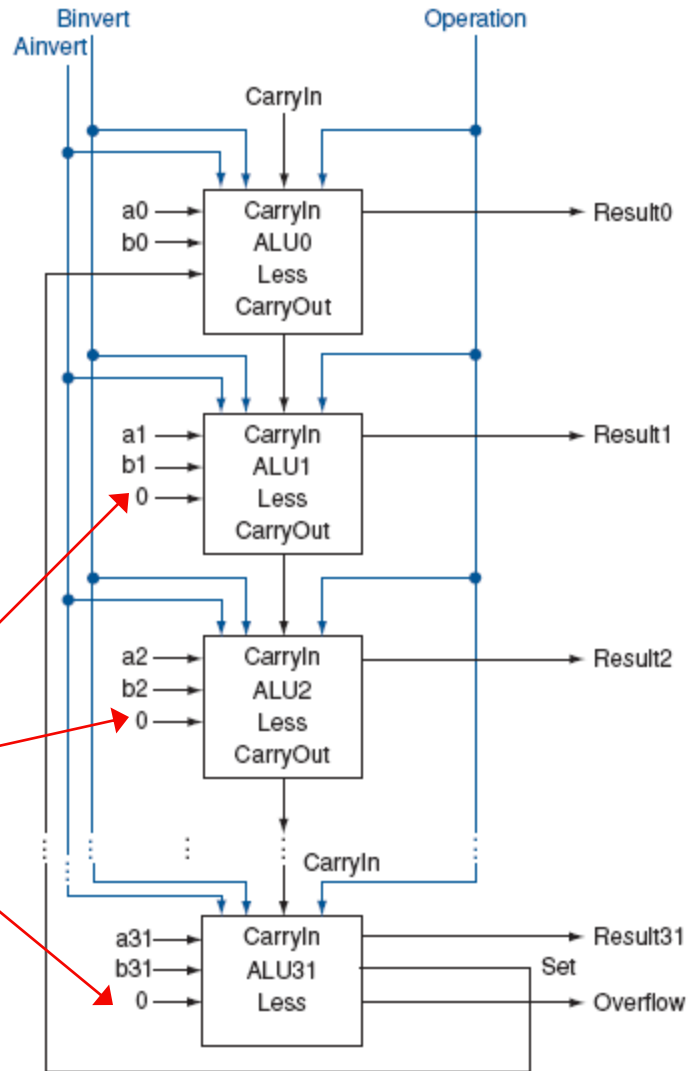

ALU hardware
for bit 32 is
special that includes
overflow detection

Test for equality

- Notice control lines:

0000 = and
0001 = or
0010 = add
0110 = subtract
0111 = slt
1100 = nor


•*Note: zero is a 1 when the result is zero!*

That is, all 32 bits are =0

Bit 1 = ainvert

Bit 2 = bnegate

Bits 3,4= op

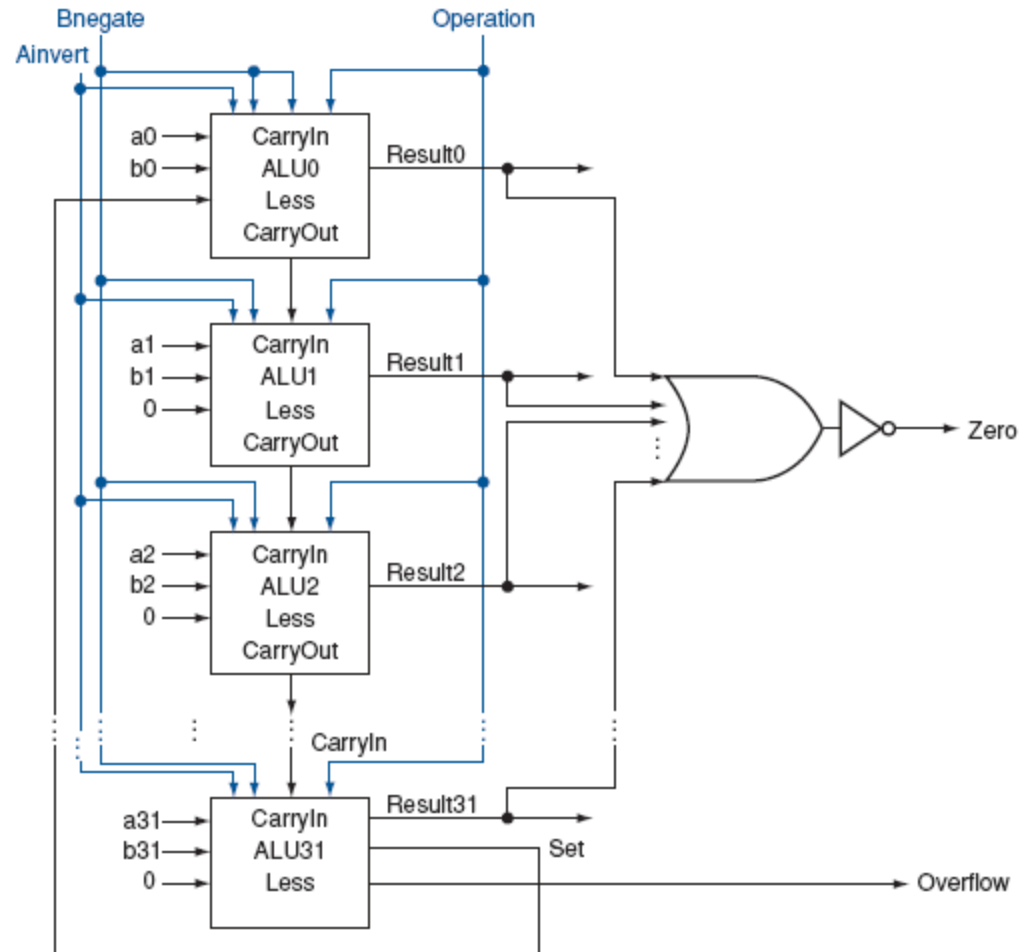

ALU in textbook: extended to include nor

- 4-bit op to ALU instead of 3 bits.
- ALU used for
 - Load/Store: F = add
 - Branch: F = subtract
 - R-type: F depends on funct field

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR


Example settings

- Control bits during add

Ainvert=0

Bnegate=Binvert=Carry

Operation=10

 


Example settings

- Control bits during subtract

Ainvert=0

Bnegate=Binvert=Carry

Operation=10

 


Example settings

- Control bits during AND

Ainvert=0

Bnegate=Binvert=Carry

Operation=00

 


Example settings

- Control bits during OR

Ainvert=0

Bnegate=Binvert=Carry

Operation=01

 


Example settings

- Control bits during NOR

Ainvert=1

Bnegate=Binvert=Carry

Operation=00

 


Example settings

- **Control bits during slt**

Ainvert=0 ← subtract

Bnegate=CarryIn=Binvert=1

Operation=11 } Select input 3 of mux

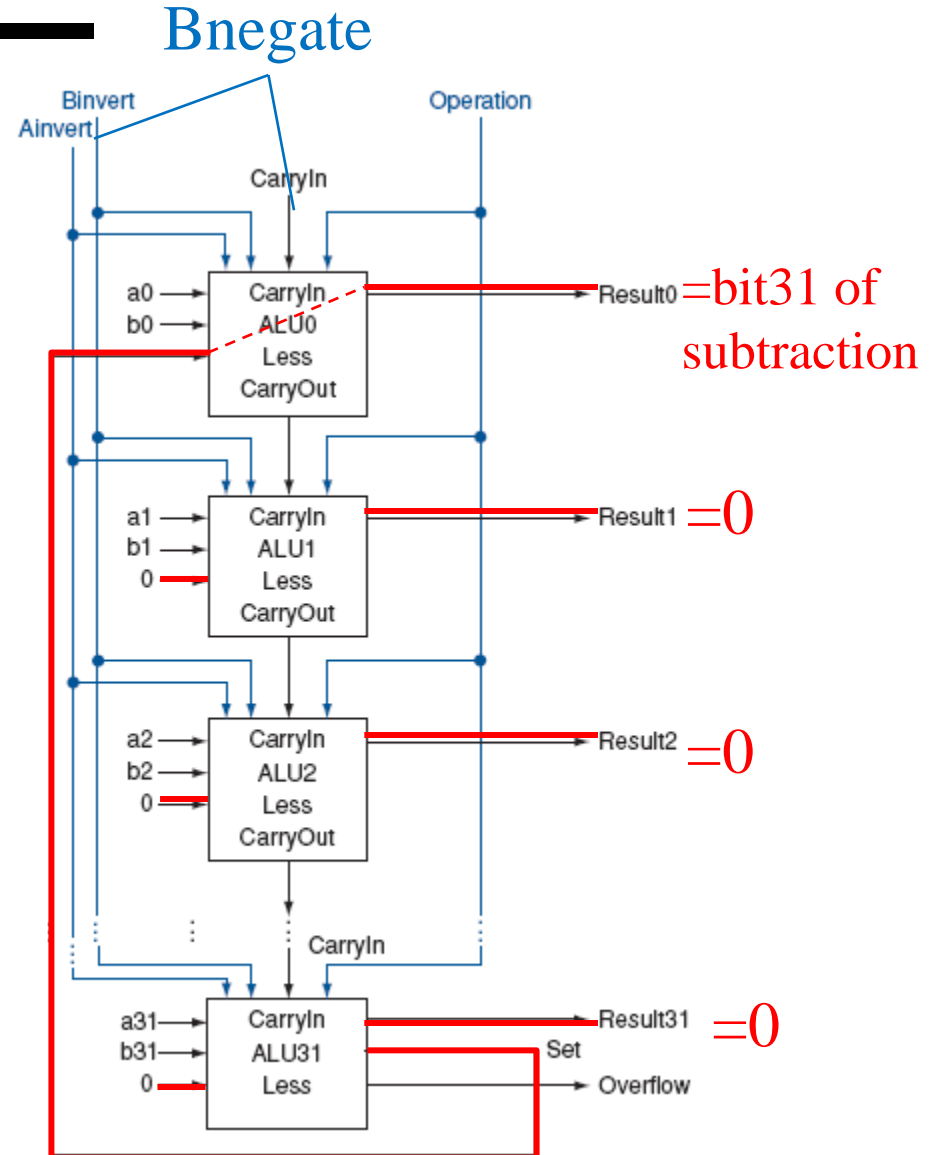

Conclusion

- We can build an ALU to support the MIPS instruction set
 - key idea: use multiplexor to select the output we want
 - we can efficiently perform subtraction using two's complement
 - we can replicate a 1-bit ALU to produce a 32-bit ALU
- Important points about hardware
 - all of the gates are always working
 - the speed of a gate is affected by the number of inputs to the gate
 - the speed of a circuit is affected by the number of gates in series (on the “critical path” or the “deepest level of logic”)
- Our primary focus: comprehension, however,
 - Clever changes to organization can improve performance (similar to using better algorithms in software):
 - E.g., Booth's algorithm for multiplication